

Ohm's Law

Practice Problems

$$\textcircled{1} \quad I = 4.7A \quad V = I \times R$$
$$R = 26\Omega \quad V = (4.7A) \times (26\Omega)$$
$$V = ? \quad V = 122.2V$$

The voltage is 122.2V

$$\textcircled{2} \quad I = 0.5A \quad V = I \times R$$
$$R = 15\Omega \quad V = (0.5A) \times (15\Omega)$$
$$V = ? \quad V = 7.5V$$

The voltage is 7.5V.

$$\textcircled{3} \quad R = 12\Omega \quad V = I \times R$$
$$I = 0.7A \quad V = (0.7A) \times (12\Omega)$$
$$V = ? \quad V = 8.4V$$

The voltage is 8.4V.

$$\textcircled{4} \quad V = 120V \quad I = V \div R$$
$$R = 34\Omega \quad I = (120V) \div (34\Omega)$$
$$I = ? \quad I = 3.53A$$

The current is 3.53A.

$$\textcircled{5} \quad R = 24\Omega \quad I = V \div R$$
$$V = 110V \quad I = (110V) \div (24\Omega)$$
$$I = ? \quad I = 4.58A$$

The current is 4.58A.

$$\textcircled{6} \quad V = 115V \\ I = 1.2A \\ R = ?$$

$$R = V \div I \\ R = (115V) \div (1.2A) \\ R = 95.8 \Omega$$

The resistance is 95.8Ω .

$$\textcircled{7} \quad I = 0.8A \\ V = 130V \\ R = ?$$

$$R = V \div I \\ R = 130V \div 0.8A \\ R = 162.5 \Omega$$

The resistance is 162.5Ω .