

9 Science (10FI)

Ohm's Law

Sample Problems:

① What is the current for a voltage of 15V and a resistance of 5Ω ?

$$\begin{array}{ll} V = 15V & I = V \div R \\ R = 5\Omega & I = 15V \div 5\Omega \\ I = ? & I = 3A \end{array}$$

The current is 3A.

② If the current is 1.20A and the resistance is 100Ω , what is the voltage?

$$\begin{array}{ll} I = 1.20A & V = I \times R \\ R = 100\Omega & V = (1.20A)(100\Omega) \\ V = ? & V = 120V \end{array}$$

The voltage is 120V.

③ If the voltage is 320V and the current is 18.5A, what is the resistance?

$$\begin{array}{ll} V = 320V & R = V \div I \\ I = 18.5A & R = (320V) \div (18.5A) \\ R = ? & R = 17.3\Omega \end{array}$$

The resistance is 17.3Ω .

Practice Problems:

1. If the current is 4.7 A and the resistance of 26Ω , what is the voltage?
2. Calculate the voltage if the current is 0.5 A and the resistance is 15Ω .
3. Calculate the voltage if the resistance is 12Ω and the current is 0.7 A.
4. Calculate the current if the voltage is 120 V and the resistance is 34Ω .
5. Calculate the current if the resistance is 24Ω and the voltage is 110 V.
6. Calculate the resistance if the voltage is 115 V and the current is 1.2 A.
7. Calculate the resistance if the current is 0.8 A and the voltage is 130 V.